
# 第4次作业

#### 10.4

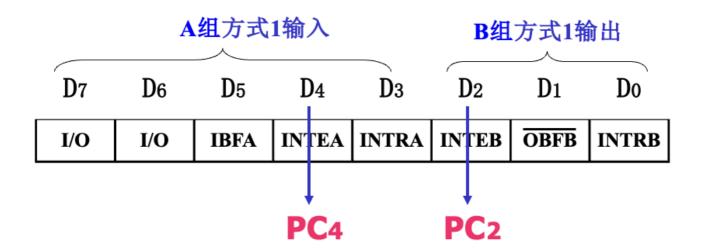10.4 设定8255A的端口A为方式1输入,端口B为方式1输出,则读取端口C的数据的各位是什么含义?



- PC0: INTEB (中断请求信号)
- PC1: ACKB (响应信号)
- PC2: INTRA (中断请求信号)
- PC3: STBA (发送信号)
- PC4: ACRA (响应信号)
- PC5: IOBFRA (输入准备就绪线控制信号)
- PC6, PC7: I/O信号


#### 10.5

- 10.5 对8255A的控制寄存器写入B0H,则其端口C的PC5引脚是什么作用的信号线?
  - 判断线带4位计数输入是否编码端点输入控制信号
  - 方式控制字为B0H = 10110000B, 说明A组为方式1输入,它将征用 PC5引脚作为输入缓冲器满信号IBFA

- 10.6 10.2.2节用8255A端口A方式0与打印机接口,如果采用端口B,其他不变,请说明应该如何修改接口电路和程序。
- 接口电路: 用端口引脚PB0~PB7与打印机DATA0~7连接, 其他不变
- 程序: 用端口B的I/O地址FFFAH替换端口A的FFF8H
- 另外,应设置端口B为方式0输出。但由于原控制字已经做到,所以无需修改

#### 10.7

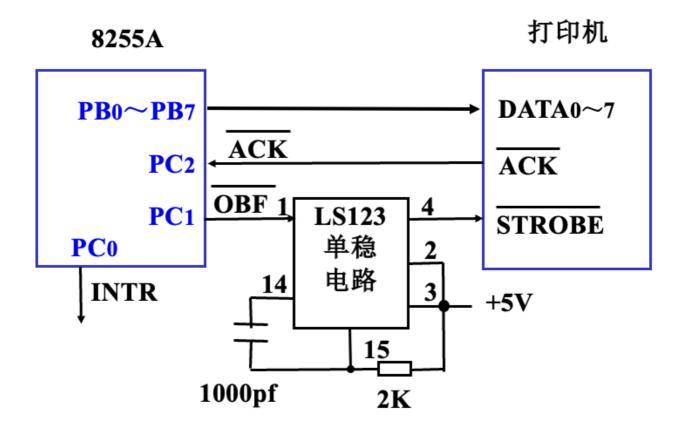10.7 10.2.3节用8255A端口A方式1与打印机接口,如果采用端口B,其他不变,请说明如何修改接口电路和程序。



```
mov dx, 0FFFEh
   mov al, 84h
   out dx, al
   mov al, 04h
   ; Set INTEB (PC2) to 0 to disable interrupt
   out dx, al
   ; . . .
   mov cx, counter ; Load the number of
bytes to print into CX
   mov bx, offset buffer; Load the address of
the string into BX
   call prints ; Call the print
subroutine
prints proc
   push ax
                   ; Save AX register
  push dx
                       ; Save DX register
print1:
   mov al, [bx]; Load a character
from the string
   mov dx, 0FFFAh
   out dx, al ; Output the character
to port B
   mov dx, 0FFFCh
print2:
   in al, dx
   test al, 02h ; Check if (PC1) is
```

## 10.8

```
;写入方式字
mov al,81h
mov dx,控制口地址
out dx,al
;使L0~L3全亮
mov al,0fh
mov dx,端口C地址
out dx,al
;控制程序段
mov dx,端口C地址
in al,dx
mov cl,4
shl al,cl
out dx,al
```

### 10.16

```
table
        db 0c0h
        db 0f9h,0a4h,0b0h,99h
        db 92h,82h,0f8h,80h
    mov dx, Offfbh
    mov al,89h
    out dx, al
again0: mov dx,0fffah
        in al, dx
        mov cx,8
        mov ah,01h
again1: shr al,1
        jnc disp0
        inc ah
        loop again1
        jmp disp1
disp0:
        mov bx, offset table
        mov al, ah
        xlat
        mov dx, 0fff8h
        out dx,al
disp1:
        mov cx,8
        mov al,01h
        mov dx, 0fff9h
disp2:
        out dx,al
        call delay
        shl al,1
        loop disp2
        jmp again0
```